
Florebencia Fils-Aime November 10, 2018


CSE 341: Computer Organization University at Buffalo


Project 2: Building an ALU


Gate Level of the one bit ALU

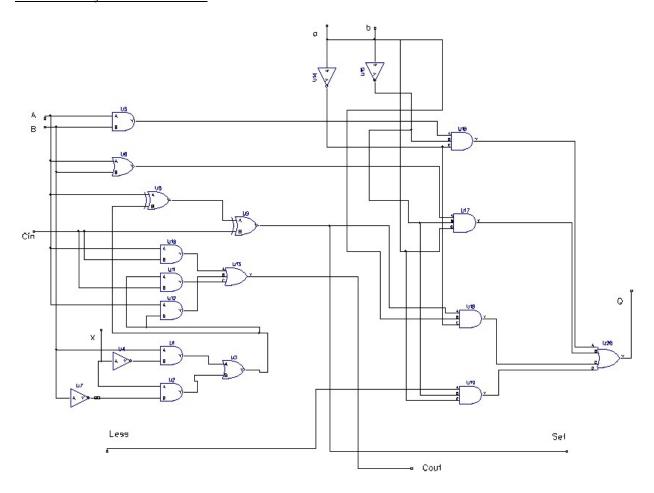


Q is the output of the 4 to 1 multiplexer. A and B are the numbers being used for arithmetic. The circuit above is the 1 bit ALU down to the gate level. The open wires a, b, and x for the opcode and their order of most significant bit is xab. For example if the opcode 110 was used then x = 1, a = 1, and b = 0. When number a is greater than or equal to number b, set less than returns a 0. If number b is greater than number a then SLT returns a 1.

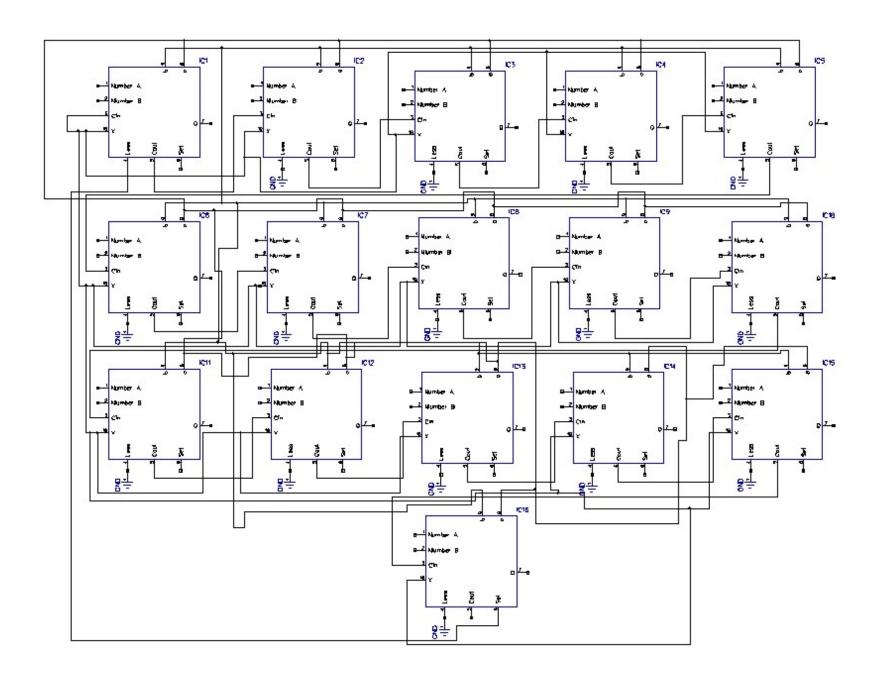

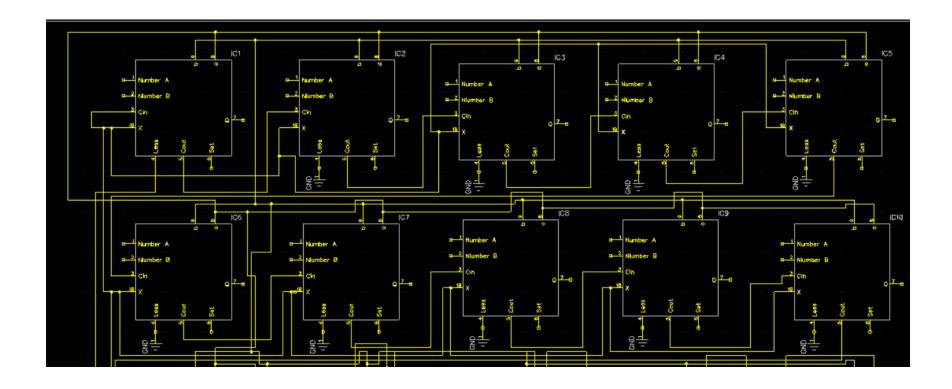

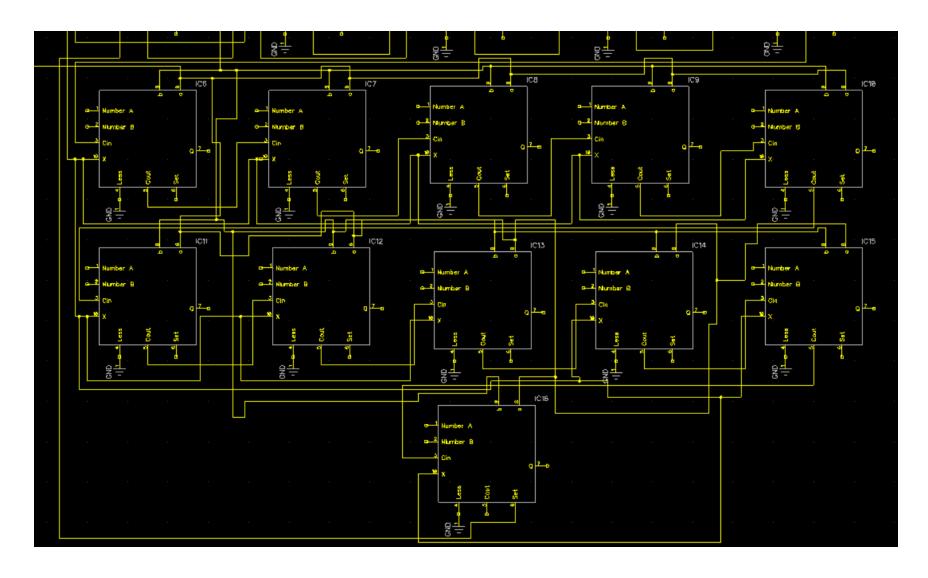


Sixteen bit ALU

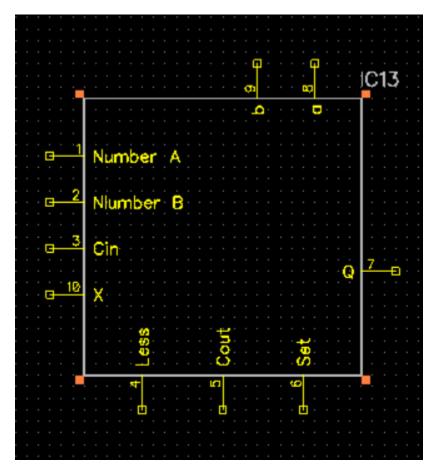

Each IC looks like this up close. The connected 16 bit ALU circuit is at the page 2. A clearer version of the schematic is at page 3 and 4. The first bit is at the top left corner. You read this from left to right and then you start on the left in the next row. All of the xs are connected. All of the as are connected. All of the bs are connected to each other. The set of the 15th bit which is at the bottom is connected to the first bit's less. This returns a set less than of one or zero since the 15th bit is the most significant. It works because set is connected to the sum part of the full adder and less is actually connected to the 4 to 1 multiplexer. All the other less ports are connected to ground because they will always pass in a zero. The Cin of the first bit is connected to the X or the most significant bit of opcode was to decide if it would add 1 or 0 depending if it was an ADD or SUB instruction.

Critical Path

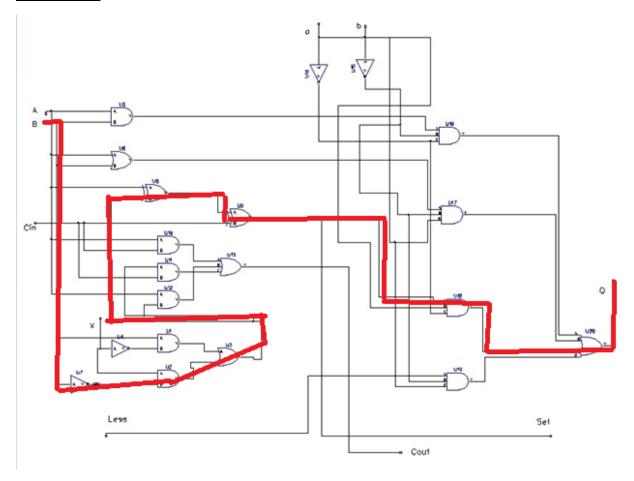

The critical path is the longest path taken by the circuit and in this case, the longest path is the SUB instruction. Since I used a 2 to 1 multiplexer, the SUB instruction is longer than the ADD instruction because of the not gate performing one's complement.

In the 1 bit ALU, the delay is 7 ns because there are seven gates along this path. In the 16 bit ALU, theoretically it should be 112 ns.

The gate cost of the ALU is how many gates are used in a circuit, so for the gate cost of 1 bit ALU is 20. For the 16 bit ALU, the gate cost is 320.

Instruction	Opcode
AND	000
OR	001
ADD	010
SUB	110
SLT	111

Zero Delay Simulation

Q is the output of the multiplexer and the s is the sum of the full adder. Choice can be ignored because it's the output of my 2 to 1 multiplexer. As you can see the 4 to 1 multiplexer is showing the right value and ADD and SUB instructions work.

Here is the values for AND and OR:

Here is the values for SLT:

When number a is greater than or equal to number b, set less than returns a 0. If number b is greater than number a then SLT returns a 1.

Unit Temporal Simulation

```
{~/CSE341 Project 2} > iverilog -t vvp alu_unit_temporal.v
timberlake {~/CSE341 Project 2} > vvp a.out > "sixteenbitunitdelay.txt"
timberlake {~/CSE341 Project 2} > cat sixteenbitunitdelay.txt
                                            z, cout=z, op=xxx, choice=zzzzzzzzzzzzzzz, q=
                                             0 a=
                                             x, cout=x, op=xxx, choice=xxxxxxxxxxxxxxxx, q=
                 20 a=
                             b=
                                    3,
                                             X
                          2,
                                       s=
                             b=
                                             22 a=
                                             x, cout=x, op=010, choice=0000000000000xx, q=
                                             x, cout=x, op=010, choice=000000000000011, q=
                 23 a=
                 24 a=
                                             x, cout=0, op=010, choice=000000000000011, q=
                                             X, cout=0, op=010, choice=0000000000000011, q=
                           2, b=
                                             5, cout=0, op=010, choice=000000000000011, q=
                 26 a=
                                             5, cout=0, op=010, choice=0000000000000011, q=
                 27 a=
                                               cout=0, op=010, choice=0000000000000011,
                  28 a=
                             b=
                                             5, cout=0, op=010, choice=00000000000000011, q=
                         123,
                             b= 5467, s=
                  40 a=
                 42 a=
                        123, b= 5467, s=
                                           124, cout=0, op=010, choice=0001010101011011, q=
                 43 a=
                        123, b= 5467, s= 126, cout=0, op=010, choice=00010101011011, q=
                        123, b= 5467, s= 5414, cout=0, op=010, choice=0001010101011011, q=
                 44 a=
                                                                                              124
                         123, b= 5467, s= 5526, cout=0, op=010, choice=0001010101011011, q=
                  45 a=
                        123, b= 5467, s= 5526, cout=0, op=010, choice=0001010101011011, q= 5414
                 46 a=
                  47 a=
                 49 a=
                         123, b= 5467, s= 5590, cout=0, op=010, choice=00010101011011,
                                    3, s= 5590, cout=0, op=110, choice=0001010101011011, q= 5590
3, s= 5591, cout=0, op=110, choice=0001010101011011, q= 5590
                 61 a=
                 62 a=
                                    3, s= 5550, cout=0, op=110, choice=11101010101010111, q= 5590
                 63 a=
                 64 a=
                                    3, s=59906, cout=0, op=110, choice=11111111111111100, q= 5550
                             b=
                 65 a=
                                    3, s=65201, cout=0, op=110, choice=11111111111111100, q= 5630
                 66 a=
                           2, b=
                                    3, s=65203, cout=0, op=110, choice=1111111111111100, q=59906
                                    3, s=64867, cout=0, op=110, choice=11111111111111100, q=65201
                 68 a=
                           2, b=
                                    3, s=64871, cout=0, op=110, choice=1111111111111100, q=65203
                                    3, s=64199, cout=0, op=110, choice=11111111111111100, q=64867
                           2, b=
                                    3, s=64207, cout=0, op=110, choice=11111111111111100, q=64871
                                    3, s=62863, cout=0, op=110, choice=11111111111111100, q=64199
                                    3, s=62879, cout=0, op=110, choice=11111111111111100, q=64207
                 72 a=
                 73 a=
                                    3, s=60191, cout=0, op=110, choice=11111111111111100, q=62863
                 74 a=
                           2, b=
                                    3, s=60223, cout=0, op=110, choice=11111111111111100, q=62879
                                    3, s=54847, cout=0, op=110, choice=11111111111111100, q=60191
                                    3, s=54911, cout=0, op=110, choice=11111111111111100, q=60223
                 76 a =
                           2, b=
                                    3, s=44159, cout=0, op=110, choice=11111111111111100, q=54847
                           2, b=
                                    3, s=44287, cout=0, op=110, choice=11111111111111100, q=54911
                 78 a=
                 79 a=
                           2, b =
                                    3, s=22783, cout=0, op=110, choice=1111111111111100, q=44159
                                    2, s=23039, cout=1, op=110, choice=11111111111111100, q=44287
2, s=45567, cout=1, op=110, choice=1111111111111100, q=22783
                           3, b=
                 80 a=
                 81 a=
```

82 a= 3,	b= 2,	s=46078,	cout=0,	op=110,	choice=1111111111111100,	q=23039
					choice=111111111111111111111111111111111111	
84 a= 3,					choice=111111111111111111111111111111111111	
85 a= 3,	b= 2,	s=51193,	cout=1,	op=110,	choice=111111111111111111111111111111111111	q=25596
86 a= 3,	b= 2,	s=53241,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=26620
87 a= 3,	b= 2,	s=36849,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=51193
88 a= 3,	b= 2,	s=40945,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=53241
89 a= 3,	b= 2,	s= 8161,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=36849
90 a= 3,	b=2,	s=16353,	cout=1,	op=110,	choice=111111111111111111111111111111111111	q=40945
91 a= 3,	b= 2,	s=16321,	cout=1,	op=110,	choice=111111111111111111111111111111111111	q= 8161
92 a= 3,	b= 2,	s=32705,	cout=1,	op=110,	choice=111111111111111111111111111111111111	q=16353
93 a= 3,	b= 2,	s=32641,	cout=1,	op=110,	choice=111111111111111111111111111111111111	q=16321
94 a= 3,	b= 2,	s=65409,	cout=1,	op=110,	choice=111111111111111111111111111111111111	q=32705
95 a= 3,	b= 2,	s=65281,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=32641
96 a= 3,	b= 2,	s=65281,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=65409
97 a= 3,	b= 2,	s=65025,	cout=0,	op=110,	choice=111111111111111111111111111111111111	q=65281
99 a= 3,	b= 2,	s=64513,	cout=0,	op=110,	choice=111111111111111101,	q=65025
100 a= 1234,	b= 5678,	s=64513,	cout=0,	op=111,	choice=111111111111111101,	q=65025
101 a= 1234,	b = 5678,	s=63489,	cout=0,	op=111,	choice=111111111111111111111111111111111111	q=64513
102 a= 1234,	b = 5678,	s=64720,	cout=0,	op=111,	choice=111111111111111111111111111111111111	q=64513
103 a= 1234,	b = 5678,	s=62672,	cout=0,	op=111,	choice=1110100111010001,	q= 1
					choice=1110100111010001,	
					choice=1110100111010001,	
108 a= 1234,	b = 5678,	s=65188,	cout=0,	op=111,	choice=1110100111010001,	q= 1
110 a= 1234,	b = 5678,	s=61092,	cout=0,	op=111,	choice=1110100111010001,	q= 1
120 a=60000,	b=50000,	s=61092,	cout=0,	op=111,	choice=1110100111010001,	q= 1
122 a=60000,	b=50000,	s= 22,	cout=1,	op=111,	choice=1110100111010001,	q= 1
· ·				-	choice=00111100101011111,	-
124 a=60000,	b=50000,	s=54386,	cout=1,	op=111,	choice=00111100101011111,	d= 0
125 a=60000,	b=50000,	s= 332,	cout=1,	op=111,	choice=00111100101011111,	
					choice=00111100101011111,	
					choice=00111100101011111,	
					choice=00111100101011111,	
				_	choice=00111100101011111,	-
					choice=00111100101011111,	
				_	choice=00111100101011111,	-
141 a= 168,					choice=00111100101011111,	
142 a= 168,					choice=00000000000000000,	
143 a= 168,					choice=00000010111111101,	
144 a= 168,				_	choice=00000010111111101,	-
145 a= 168,					choice=00000010111111101,	
146 a= 168,				_	choice=00000010111111101,	-
147 a= 168,					choice=00000010111111101,	
148 a= 168,				_	choice=00000010111111101,	-
160 a= 168,					choice=00000010111111101,	
162 a= 168,					choice=00000010111111101,	
200 a= 168,	7 7 7 7				choice=00000010111111101,	$\alpha = 765$

Time Start and Finish of Each Instruction in nanoseconds								
	Instructions							
	ADD	SUB	AND	OR	SLT			
start	20	60	140	160	100			
end	28	79	148	162	110			
start	40	80	Σ	120				
end	49	99		130				

X means not tested.

On each gate, I put a delay of one nanoseconds. There were eight tests done to analyze the temporal dependence of the delay. There were two add instructions, two sub instructions, one and instruction, one or instruction, and one slt instruction. The blue boxes contain ADD instructions, the purple boxes contain SUB instructions, the green boxes contain SLT instructions, the red box contains an AND instruction and the rest is an OR instruction.

An ADD instruction takes 8 to 9 ns to run. A SUB instruction takes 19 ns to run. An AND instruction takes 8 ns to run, and an OR instruction takes 2 ns. The SLT instruction takes 10 ns to run. They all take a different amount of time to run and they start at different times so that it is easier to see.

Analysis of the Average Delay

The average delay across all 1000 samples came out to be 7 ns which is the same value as the critical delay.